

1.4.3 Boolean Logic Questions

a. Complete the following truth table for the XOR gate.

Input A	Input B	Output Q
0	0	
0	1	
1	0	
1	1	

[1]

b. Draw logic circuits for the following Boolean expressions:


i.
$$Q = A \underline{v} B v \neg B$$

ii.
$$Q = \neg A \land B \lor C$$

iii.
$$Q = \neg(A \lor B) \lor (A \land C)$$

[3]

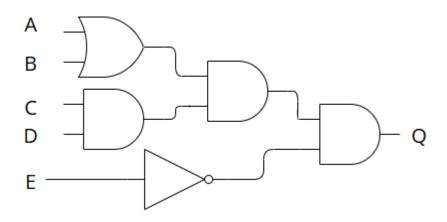2. The Figure below shows a logic circuit.



a. Write the equivalent Boolean expression.

[4]

b. What are the values of F, G, H, K & Q if A, B, C, D & E are all equal to 1?

[5]

3. Three sensors A, B & C are used to monitor a process. A signal X is output from the circuit. X has the value 1 if either of the following condition are met:

Sensor A outputs 1 AND sensor B outputs 0 Sensor B outputs 1 OR sensor C outputs 0 Draw a logic circuit to represent these conditions.

[5]